

DECEMBER 2014

**P/ID 17454/
RCD/PCAG**

Time : Three hours

Maximum : 75 marks

PART A — (5 × 5 = 25 marks)

Answer ALL questions.

1. (a) Convert the following:

(i) $(0.6875)_{10} = (?)_2$

(ii) $(673.124)_8 = (?)_2$

(iii) $(306.D)_{16} = (?)_2$.

Or

(b) Use 2's complement to perform $M - N$ with the given binary numbers.

(i) $1010100 - 1000100$

(ii) $1000100 - 1010100$.

2. (a) Draw the circuit of full-Subtractor and explain.

Or

(b) Explain the operation of a multiplexer with its function table.

3. (a) Draw the logic diagram of D flip-flop and explain its working principle.

Or

- (b) Explain the sequential circuit that uses a register.

4. (a) Write short notes on scratchpad memory.

Or

- (b) Write short notes on the design of arithmetic circuit.

5. (a) Explain briefly the design of the Hard-wired control.

Or

- (b) Write short notes on microprogram control.

PART B — (5 × 10 = 50 marks)

Answer any FIVE questions.

6. Simplify the Boolean function using K-Map method $F(w,x,y,z) = \sum (0,1,2,4,5,6,8,9,12,13,14)$.
7. Discuss on various logic gates with their truth tables.
8. Explain the multilevel NAND circuits.

9. Describe a four bit ripple counter and its working procedure with a neat circuit and Timing diagram.
 10. Explain the JK flip-flop with a neat diagram.
 11. Discuss on the status register in detail.
 12. Draw the block diagram of digital computer and explain the various registers.
 13. Explain memory-reference instructions with examples.
-