

MAY 2015

P/ID 17502/PCASB

Time : Three hours

Maximum : 100 marks

PART A — ($6 \times 5 = 30$ marks)

Answer any SIX questions.

1. Write the first 20 decimal digits in base 3.
2. Convert the following decimal numbers to binary :
 - (a) 12.0625
 - (b) 10^4
 - (c) 673.23
 - (d) 1998.
3. Give the truth table of a 3-to-8 line decoder.
4. Describe ROM with a block diagram.
5. Describe clocked JK flip-flop.
6. Write about clocked RS flip-flop.
7. Give the block diagram of a processor unit.
8. Describe the block diagram of a PLA control.

PART B — (7 × 10 = 70 marks)

Answer any SEVEN questions.

9. Obtain the 9's and 10's complement of the following decimal numbers :
 - (a) 13579
 - (b) 09900
 - (c) 90090
 - (d) 10000
 - (e) 00000.
10. Summarize the basic theorems and properties of Boolean algebra.
11. Illustrate the steps required in PLA implementation.
12. Describe a 4-to-1 line multiplexer.
13. Explain edge-triggered flip-flop.
14. Illustrate a 4 bit binary ripple counter.
15. Explain the process of a shifter.
16. Describe scratch pad memory.
17. Explain timing and control in computer design.
18. Describe the micro program control unit for computer.