

MAY 2011

P/ID 17454/RCD/PCAG

Time : Three hours

Maximum : 75 marks

PART A — (5 × 5 = 25 marks)

Answer ALL questions.

All questions carry equal marks.

1. (a) What is a number system? List the advantages of binary number system. With an example discuss how a decimal number can be converted into octal number.
Or
(b) What is Boolean Algebra? Discuss the basic properties of Boolean Algebra.
2. (a) What is a combinational circuit? Implement a half adder using AND and OR gates.
Or
(b) What is a multiplexer? With a circuit diagram discuss its function.
3. (a) What is an excitation table? Develop the excitation table of a JK flip-flop.
Or
(b) What is a state equation? Discuss with an example.

4. (a) What is a scratch pad memory? Discuss.

Or

(b) Write a short note on microprogramming.

5. (a) What is an instruction set? Discuss.

Or

(b) What is an instruction? Write a short note on the execution of an instruction.

PART B — (5 × 10 = 50 marks)

Answer any FIVE questions.

All questions carry equal marks.

6. Write a short note on Integrated circuits.

7. Using tabulation method simplify

$$f(a, b, c, d) = \sum_m (0, 2, 4, 7, 9, 11, 15) + \sum_d (3, 8, 12)$$

Verify the results using karnaugh map.

8. What is a decoder? Design a 3 to 8 line decoder and implement it using AND and OR gates.

9. Discuss the working of a Bidirectional shift register with parallel load.

10. Design a binary up-down counter and discuss its function.

2 P/ID 17454/RCD/PCAG

11. Write a short note on the design of arithmetic circuit.
 12. Draw the detailed block diagram for computer and discuss.
 13. Discuss on the following:
 - (a) PLA control.
 - (b) H/W control.
-

3 P/ID 17454/RCD/PCAG